

Sheet (4) : Analog ICs ELE322
MOS-Differential and BiCMOS Amplifiers



1. Consider the MOS differential pair shown in figure (1) with gate of Q2 grounded. Let $\mu_n C_{ox} = 20 \mu A/V^2$, $V_t = 1V$, $W/L = 20$, and $I = 16 \mu A$. Find v_{GS1} , v_{GS2} , v_S , and v_{G1} that correspond to the following distributions of the current I between Q_1 and Q_2 :
 - a- $i_{D1} = i_{D2} = 8 \mu A$
 - b- $i_{D1} = 12 \mu A$ and $i_{D2} = 4 \mu A$
 - c- $i_{D1} = 16 \mu A$ and $i_{D2} = 0 \mu A$ (Q_2 is just cuts off.)Confirm that the value of v_{G1} obtained in (c) is the same as found using the equation given in lectures.
2. An NMOS differential amplifier utilizes a bias current of $8 \mu A$. The devices have $V_t = 1V$, $W = 60 \mu m$, and $L = 6 \mu m$, in a technology for for which $\mu_n C_{ox} = 20 \mu A/V^2$. Find V_{GS} , g_m , and the value of v_{id} for full current switching. To what value should the bias current be changed in order to double the value of v_{id} for full current switching.
3. Design the MOS differential amplifier of figure (1) to operate at $V_{GS} - V_t = 0.2 V$ and to provide a transconductance g_m of $0.1 mA/V$. Specify the W/L ratios and the bias current. The technology available provides $V_t = 1V$ and $\mu_n C_{ox} = 20 \mu A/V^2$.
4. An NMOS differential pair is to be used in an amplifier whose drain resistors are $100 k\Omega \pm 1\%$. For the pair $K = 100 \mu A/V^2$ and $V_t = 1V$. A decision is to be made concerning the bias current to be used, whether $100 \mu A$ or $200 \mu A$. For differential output, contrast the differential gain and input offset voltage for the two possibilities.
5. An NMOS amplifier, whose designed operating point is with V_{GS} one-half volt above the nominal 1-V threshold, is suspected to have a variability of V_t , K , and R_D (independently) of $\pm 5\%$. What is the worstcase input offset voltage you would expect to find? What is the major contribution to this total offset? If you used a variation of one of the drain resistors to reduce the output offset to zero and thereby compensate for uncertainties (including that of the other R_D), what percentage change from nominal value would you require? If by selection you reduced the contribution of the worst case of the offset by a factor of 10, what change in R_D would be needed?
6. For the simple MOS mirror shown in figure (2) the devices nominally have $K = 100 \mu A/V^2$ and $V_t = 1V$. Measurement with $V_{DS2} = V_{DS1}$ and $I_{REF} = 1 mA$ shows the output current to be 5% low. It is assumed that Q_2 differs from Q_1 in one or more ways. If the difference in current is all due to K_2 being different from K_1 , find what this difference must be. If, on the other hand, the difference in current is all due to V_{t2} being different from V_{t1} , find what this difference must be.

 


Figure (1)

 


Figure (2)

- 7 What W/L ratio must a MOSFET have in order to have a g_m equal to that of a BJT when both are biased at a current I of $100\ \mu\text{A}$. Comment on the results
 - 8 If the parameter λ of a MOSFET is approximately inversely proportional to the channel length L , how do r_o and the intrinsic voltage gain change with L ?
 - 9 How does the thickness of the gate oxide affect the intrinsic gain of the common-source amplifier? Discuss the trade-offs that have to be considered in deciding on oxide thickness?
- Hint: If not stated otherwise consider for BJTs: $V_A = 50\text{V}$ and $\beta = 100$; and for MOSFETs: $L = 2\ \mu\text{m}$, $\lambda = 0.05\text{V}^{-1}$, $|V_t| = 1\text{V}$, and $\mu_n C_{ox} = 20\ \mu\text{A/V}^2$.**