



Alexandria University

Faculty of Engineering

Electrical Engineering Department

EE431: Digital Integrated Circuits

Sheet 5: Sequential MOS Logic Circuits

- 1) Consider the monostable multi-vibrator circuit drawn in Figure 1. Calculate the output pulse width.

$$V_T(\text{dep}) = -2 \text{ V}$$

$$V_T(\text{enh}) = 1 \text{ V}$$

$$k' = 20 \mu\text{A}/\text{V}^2$$

$$Y = 0$$

 


Figure 1

- 2) Shown in Figure 2 is an NMOS Schmitt trigger. Draw the voltage transfer characteristic. Include values for all important points on the graph. Use the parameters in Problem 1 and $\lambda = 0$. W/L ratios for the transistors are given below.

	M1	M2	M3	M4
W/L	1	0.5	10	1

 


Figure 2

- 3) Design a circuit to implement the truth table shown in Figure 3. A gate-level design is sufficient.

S	R	Q	\bar{Q}
0	1	1	0
1	0	0	1
1	1	Q	\bar{Q}

 


Figure 3

- 4) The circuit you have designed in Problem 3 is embedded in the larger circuit shown in Figure 4. Complete the timing diagram for the output.

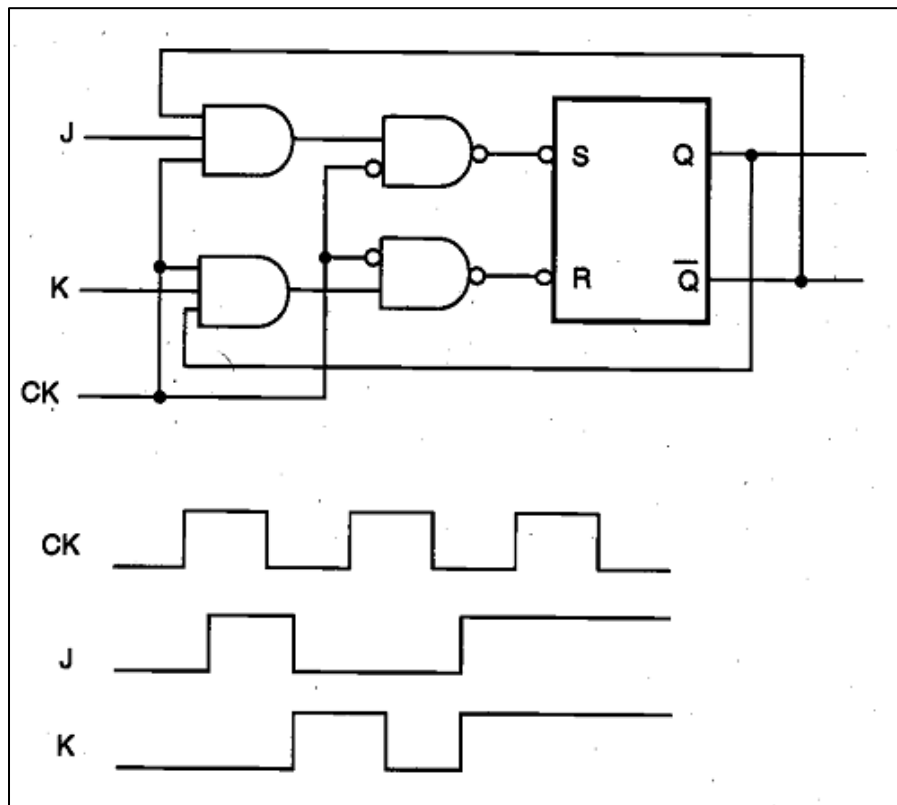


Figure 4

- 5) The voltage waveforms shown below (in Figure 5) are applied to the NMOS JK master-slave flip-flop shown in Figure 6. With the flip-flop initially reset, show the resulting waveforms at nodes Q_m (master flip-flop output) and Q_s . (slave flip-flop output).

 


Figure 5

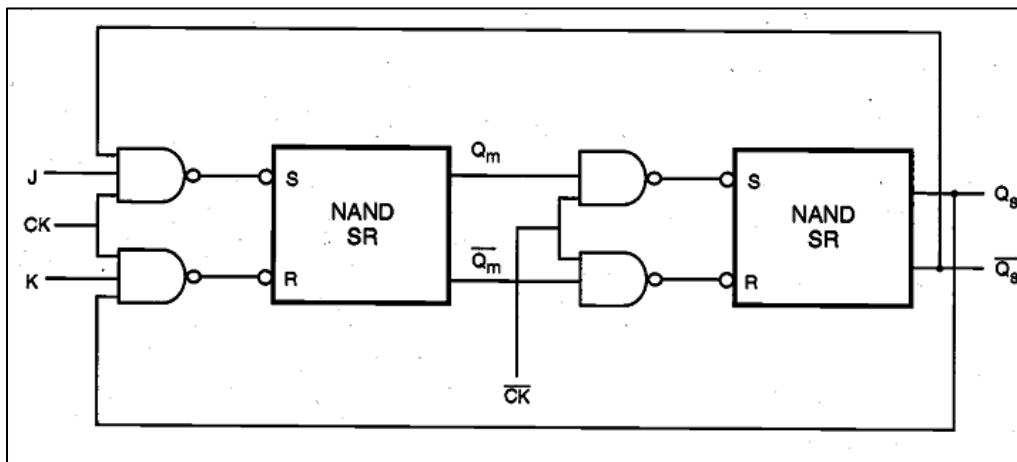


Figure 6